

# EE5331-DSP Architectures and Embedded Systems

## Programming Assignment 3

### 1 Introduction

In this assignment, we will implement a 4-bit Johnson counter and a timer on the FPGA board.

### 2 Implementing a Johnson Counter on an FPGA

In the first part of this assignment, we will implement a Johnson counter. A 4-bit Johnson counter is shown in Fig. 1. The Johnson counter is like a ring counter, however, the inverted output of the last flip-flop is connected to the input of the first flip-flop. A 3-bit Johnson counter will have states given by 000, 100, 110, 111, 011 and 001 and this sequence repeats.

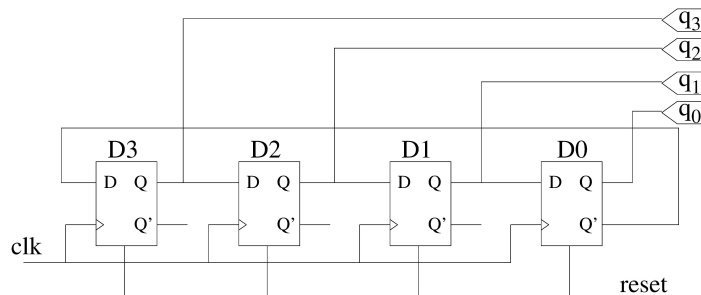


Figure 1: 4-bit Johnson counter

**Task :** Implement a 4-bit Johnson counter on the FPGA. You need to write a clock divider program and create an appropriate ucf file. The output for the Johnson counter should appear on LEDs on the FPGA board. Partial Verilog programs for some of the other parts are given below.

```
module johnson4bit(q3,q2,q1,q0,clk,rst);
input clk, rst;
output q0,q1,q2,q3;
wire q3bar, q2bar, q1bar, q0bar;
dflopflipflop_withreset D3(q3,q3bar,---,rst,clk);
dflopflipflop_withreset D2(q2,q2bar,---,rst,clk);
dflopflipflop_withreset D1(q1,q1bar,---,rst,clk);
dflopflipflop_withreset D0(q0,q0bar,q1,rst,clk);
endmodule
```

```
module dflopflipflop_withreset(q, qbar, d, rst, clk);
output q,qbar;
input d, rst, clk;
reg q,qbar;
always @ (posedge clk)
begin
if (~rst)
begin
q <= 1'b0;
qbar <= 1'b1;

```

```

    end
  else
    begin
      q <= ----; // complete the description of f/f
      qbar <= ----; // A Johnson counter transfers whatever is at
    end // q to the data i/p of next f/f except for the leftmost
  end // f/f whose i/p is qbar from the rightmost f/f
endmodule

```

- Write a clock divider module in Verilog

### 3 Timer Implementation on an FPGA

Embedded systems typically include a *timer* in some form (implemented using a microcontroller or other platforms). Here we will design a timer in Verilog and implement it on the FPGA. For this purpose, we will use the sliding switches and LEDs on the Xilinx Starter Kit as shown in Figure 2.

 


Figure 2: Starter Kit's LEDs to be used for display of seconds, minutes and hours

**Task:** Complete the following program to display a digital clock. When *start* is set to 0, initialization of the block (which includes *count*) is done. When *start* is 1, the *clock operation* must be performed (and displayed on the FPGA board). Write a *.ucf* file, take input from a sliding switch on the FPGA board and direct the output on (to) the LEDs.

```

module digital_clock_1Hz(start, clk, sec, minutes, hours);

input start;
input clk;

```

```

output sec;
output reg [5:0]minutes;
output reg hours;

reg [.....]count = .....; // fill in size of count to generate a 1-Hz clock
reg clk_1Hz = 1'b1, clk_60sec = 1'b1 ;
reg [5:0]sec_count;

assign sec = clk_1Hz;

// 1-second clock generating block

always@(posedge clk)
begin

    if(start == 1'b0)
    begin
        count <= .....;
        clk_1Hz <= !clk_1Hz ;
    end
    else
    begin
        if(count == ..... ) // fill appropriate count to generate a 1-second clock

        begin
            count <= ..... ;
            clk_1Hz <= !clk_1Hz;
        end
        else
        count <= count + 1'b1;
        end
    end

end

//1-minute clock generating block

always@(posedge clk_1Hz)
begin
    if(start == 1'b0)
    begin
        sec_count <= 6'd0;
        clk_60sec <= !clk_60sec;

    end
    else
    begin
        if(sec_count == ..... ) // fill appropriate value for count to generate a 1-minute clock
        begin
            sec_count <= 6'd0;
            clk_60sec <= ..... ;
        end
        else
        sec_count <= .....;
        end
    end

end

```

```

// minutes and hours counting block

always@(posedge clk_60sec)
begin
    if(start == 1'b0)
begin
minutes <= 6'd0;
hours <= 1'b0 ;
end
    else
begin
if(minutes == ..... ) // fill in to generate increment for "hour"
begin
minutes <= 6'd0 ;
hours <= .....;
        end
    else
minutes <= .....;
end

end

endmodule

```